

NEISSE - ELEKTRO 2000

Name:


1	2	3	4	5	Σ

Tasks for the finale
90 min ; with formulary (english edition)

1

$U_a = 12V$
 $U_b = 10V$
 $R_1 = 10\Omega$
 $R_2 = 20\Omega$
 $R_3 = 5\Omega$

Calculate the voltages $U_1, U_2, U_3!$

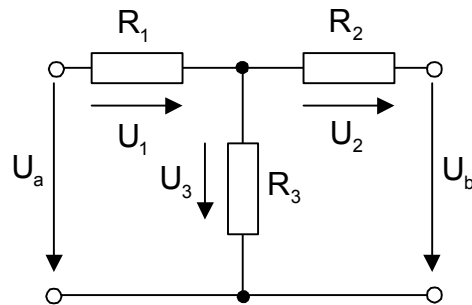


2

$R_1 = 10k\Omega$
 $U_1 = 10V; U_2 = 1V;$
 $U_3 = 0.1V; U_4 = 0.01V$

a)
Calculate the values of $R_2; R_3; R_4!$

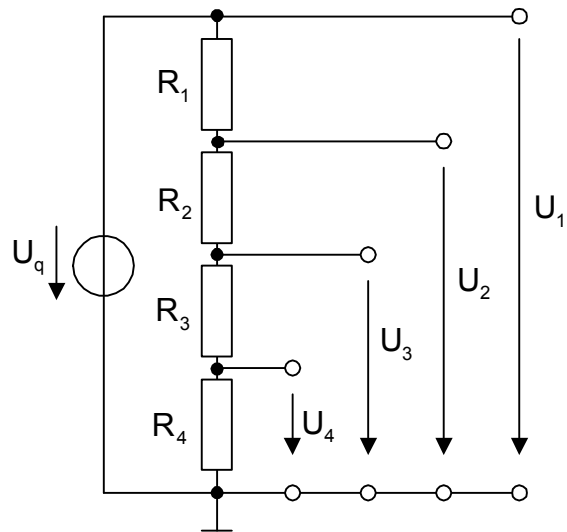b)
Calculate the resistor, that loads the voltage source!




3

The circuit is supplied by ac voltage (frequency $f = 50\text{Hz}$). The measuring instruments show:

$$U = 48\text{V} \quad I = 2,2\text{A} \quad P = 79,2\text{W}$$

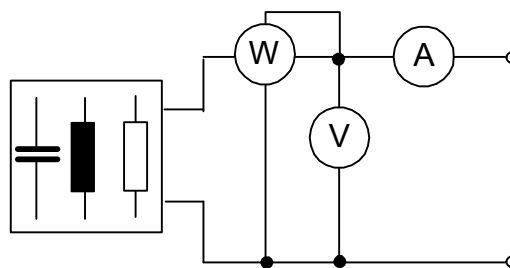
Describe the behavior of the circuit with the help of 2 electronic devices and calculate their values!



4

A sheet of paper ($\epsilon_r = 2,3$) is put into a plate capacitor (area $A = 0,4\text{m}^2$, distance $d_1 = 3\text{mm}$, permittivity (vacuum) $\epsilon_0 = 8,85 \cdot 10^{-12} \text{As/Vm}$). The measured capacity is $C = 4,0\text{nF}$.

Calculate the thickness d of the paper!

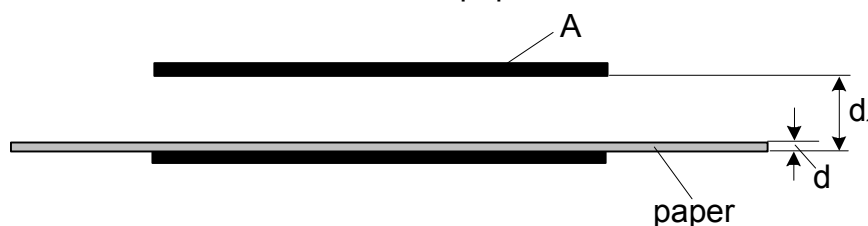

5

The magnetic flux Φ in the given iron core is produced by the field coil (number of windings N_0) with current i :

$$\Phi(t) = 20 \cdot 10^{-4} \text{Vs} \cdot \sin \omega t$$

with frequency $f = 50\text{Hz}$

$$N_0 = 200 \quad N_1 = 10 \quad N_2 = 20$$

$$N_3 = 33 \quad N_4 = 4$$

a)

Calculate the magnetic resistor R_m of the iron core. The current in the field coil is given by:

$$i = 20\text{mA} \cdot \sin \omega t$$

b)

Calculate the voltages u_{ab} , u_{cd} , u_{ef} and u_{gh} !

