

# NEISSE - ELEKTRO 2000

Name: .....

1	2	3	4	5	6	S

Tasks for the finale test  
90 min ; with formulas (english edition)

**1**


The following circuit is given (figure).  
The resistance  $R_X$  is setting to fulfill the  
condition:  $U_X = 0,1U$

Calculate the value of  $R_X$ !

$$R_1 = 1\text{k}\Omega$$

$$R_2 = 2\text{k}\Omega$$

$$R_3 = 3\text{k}\Omega$$

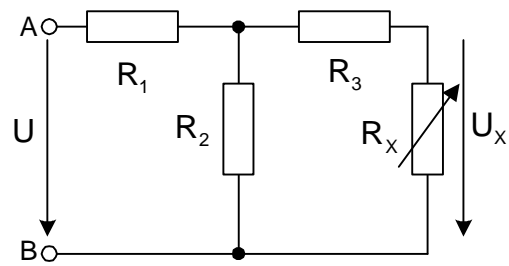


**2**

The following circuit is given (figure).

$$C_1 = 5\ \mu\text{F} \quad C_2 = 1\ \mu\text{F}$$

$$R_1 = R_2 = R_3 = 1\ \text{M}\Omega$$

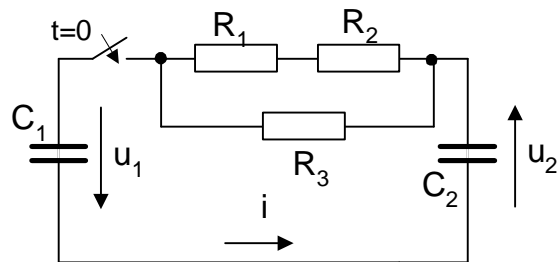
The capacitor  $C_1$  is charged up to a  
voltage  $U_1 = 200\ \text{V}$ . The circuit breaker  
is closed in the moment  $t = 0$ .



- Calculate the values of the voltages  $u_1$  and  $u_2$  for the condition  $t \gg 0$ !
- Calculate the total energy stored in the capacitors for the moments  $t < 0$  and  $t \gg 0$ !
- Calculate the value of the electric current in the moment after closing the circuit breaker.
- Calculate the time constant of the switching operation!

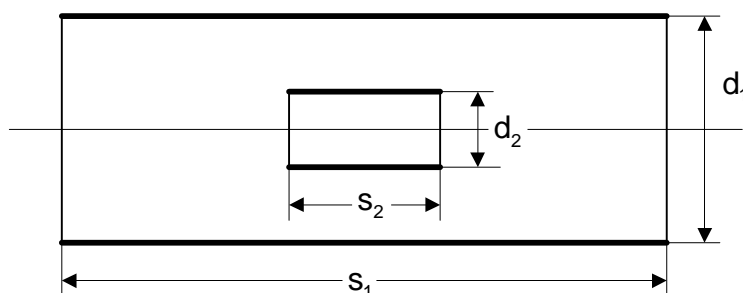**3**

A small cylindrical coil 2 ( $s_2 = 15\text{cm}$ ;  $d_2 = 3\text{cm}$ ;  $N_2 = 100$ ) is situated in the middle of a  
long cylindrical air-core coil 1 ( $s_1 = 1\text{m}$ ;  $d_1 = 8\text{cm}$ ;  $N_1 = 800$ ).




Coil 1 is connected to AC  
voltage  $u_1$ :  
 $u_1 = 100\text{V} \cdot \cos(2\pi \cdot f \cdot t)$  with  
 $f = 50\text{kHz} = 50000\text{Hz}$

Calculate the peak value of the voltage  $\hat{u}_2$  measurably on the circuit points of the  
coil 2!

4

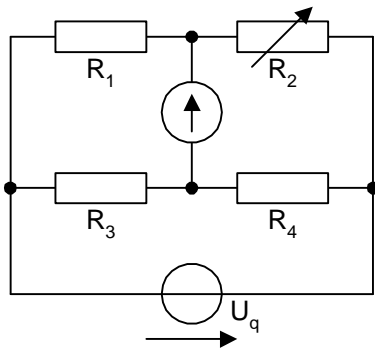The following bridge circuit is given (figure).



$$R_1 = 200 \, \Omega;$$

$$R_3 = 100 \, \Omega$$


$$R_4 = 130 \, \Omega$$

The maximum load for all of the resistors is given by  $P_{\max} = 1 \, \text{W}$

- Calculate the resistor  $R_2$  for the bridge balance!
- Calculate the maximum permissible value of the voltage  $U_q$  in case of bridge balance!

5

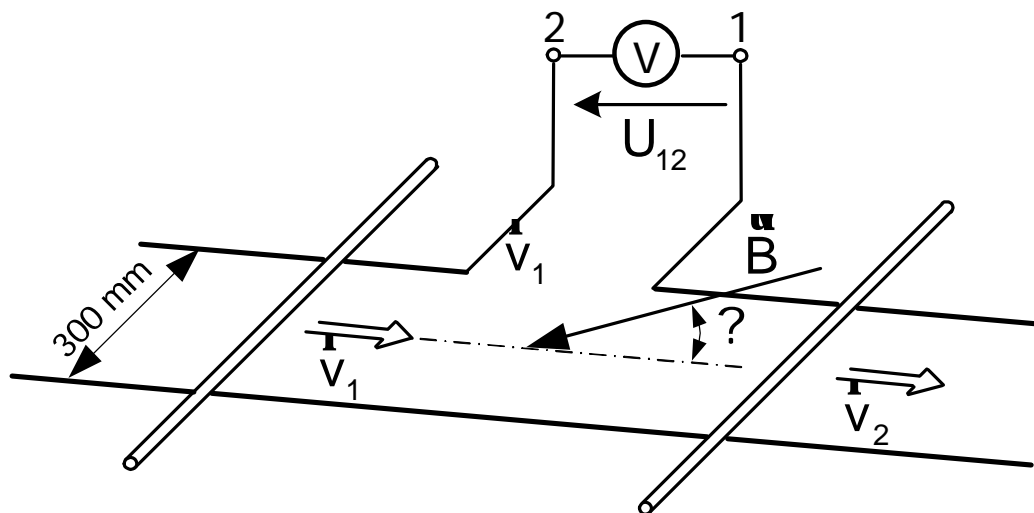A homogeneous magnetic field  $B = 0.2 \, \text{T}$  with down grade of  $\beta = 20^\circ$  against the plane of the both rails. On the rails are moved two metallic rods - always in contact with the rails - with the velocity  $v_1 = 0.2 \, \text{m/s}$  and  $v_2 = 0.5 \, \text{m/s}$ .



Calculate the voltage  $U_{12}$  indicated by the measurement device. The loop resistance of the measuring circuit is given by  $R_s$ , the internal resistance of the voltage meter is given by  $R_M$ . It is imperative:  $R_M \gg R_s$ !