

NEISSE - ELEKTRO 2000

Name:

1	2	3	4	5	Σ

Tasks for the finale test
90 min; with formula sheet (English edition)

1

Given is the electrical circuit according to figure 1

$$R_1 - R_7 = 10 \Omega$$

$$U_{q1} - U_{q4} = 2 \text{ V}$$

$$R_{i1} - R_{i4} = 1 \Omega$$

- Simplify the circuit in figure 1 to a basic circuit with only one voltage source and one load resistance
- Calculate for the basic circuit the parameter U_q , R_i , R_a , I and U_{AB}
- Calculate the amounts of all currents from I_1 to I_7 and all voltages from U_1 to U_7 !

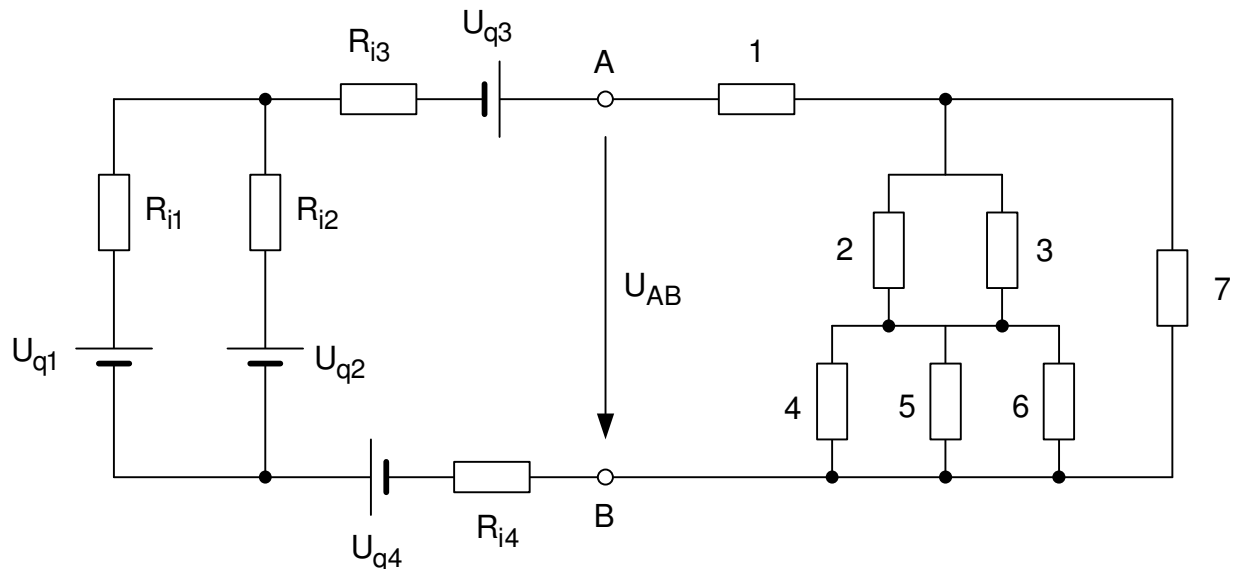


Figure 1

2

An electrical current of $I = 100 \text{ A}$ is flowing through a conductor consisting of three different materials in series connection like shown in figure 2 a)

The conductivity of the materials is: $\kappa_1 = 1 \text{ S/cm}$ $\kappa_2 = 2 \text{ S/cm}$ $\kappa_3 = 4 \text{ S/cm}$

- Calculate the voltage $U_1 - U_3$ over each material part!
- Calculate the electrical field intensity $E_1 - E_3$ over each material part!

The same current of $I = 100 \text{ A}$ is flowing through a conductor consisting of three different materials in parallel connection like shown in figure 2 b).

The conductivity of the materials is the same as in figure 2 a).

- c) Calculate the different currents $I_1 - I_3$ and the voltage!
 d) Calculate the current density $S_1 - S_3$ in each material part!

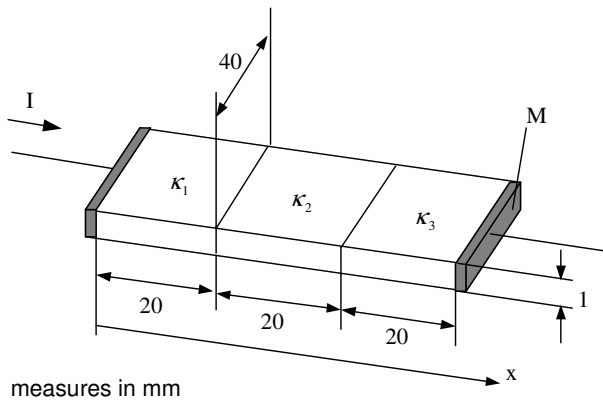


Figure 2a

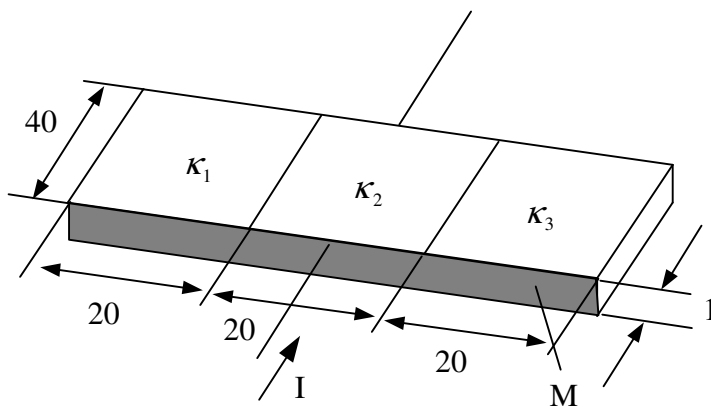


Figure 2b

3

The determination of the resistance R is done by two different measurements. The first one (figure 3a), exact for the voltage, with the results $U = 9,0 \text{ V}$ and $I = 76 \text{ mA}$ under consideration of a resistance of the voltage meter $R_{\text{MU}} = 9,0 \text{ k}\Omega$. The second one (figure 3b), exact for the current, with the results $U = 10,0 \text{ V}$ and $I = 80 \text{ mA}$.

Calculate the resistance R and the resistance of the current meter R_{MI} .

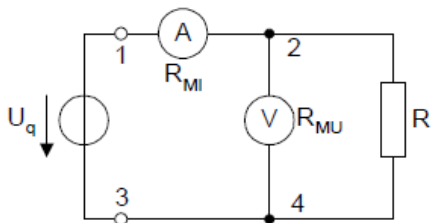


Figure 3a

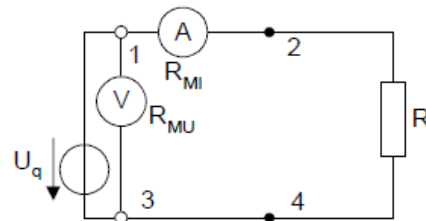


Figure 3b

4

A high voltage cable with a two layer insulation according to figure 4 can be considered as two cylindrical capacitors with the following parameters:

$U_{\text{total}} = 10 \text{ kV}$, $f = 50 \text{ Hz}$

length of the cable $l = 100 \text{ m}$

$r_a = 4 \text{ cm}$

$r_i = 1 \text{ cm}$

$r_1 = 2 \text{ cm}$

$\epsilon_{r1} = 3$

$\epsilon_{r2} = 1$

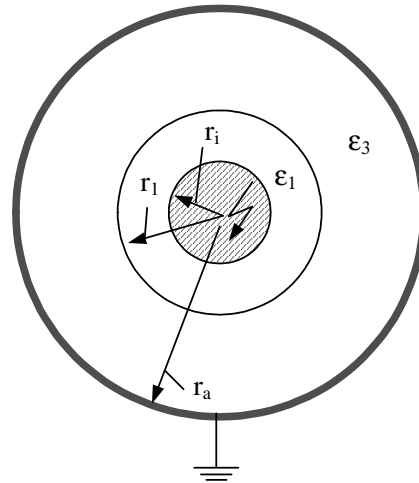


Figure 4

- Calculate the capacitances C_{total} , C_1 and C_2 of this cable!
- Calculate the electrical charge $Q = Q_1 = Q_2$ of this cable!
- Calculate the voltage over each layer of the insulation U_1 and U_2 !

5

The current in an unlimited long conductor is $I = 1000 \text{ A}$

- Calculate the magnetic field strength H for a straight conductor like indicated in figure 5 a) in three different points P_1 , P_2 and P_3 ($r = 0,5 \text{ m}$).
- Calculate the magnetic field strength H for a right angle conductor like indicated in figure 5 b) in three different points P_1 , P_2 and P_3 .
- Calculate for b) the magnetic flux density B in P_1 if the conductor is surrounded by air.

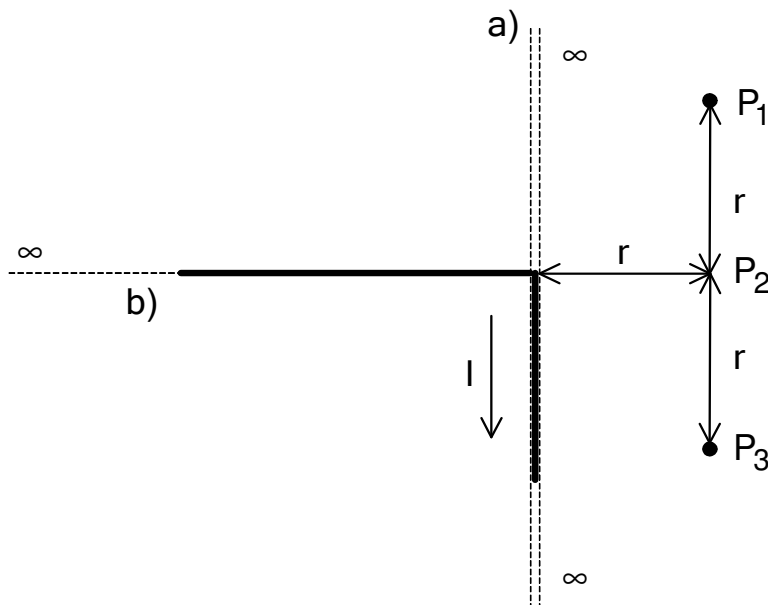


Figure 5