

| | 1 | 2 | 3 | 4 | 5 | Σ |
|-------|---|---|---|---|---|---|
| Name: | | | | | | |

Tasks fort he finale test 90min ; with formula sheet (English edition)

1

Given is the electrical circuit according to figure 1



Figure 1

Calculate the amount of R_{ab} and the amounts of all currents from I_1 to I_8 and all voltages from U_1 to U_8 .

2

Calculate the values of the current I_2 and the current $\mathsf{I}_4\,$ for the electrical circuit according to figure 2

 $R_1 = 1 \ \Omega \qquad R_2 = 1,5 \ \Omega \qquad R_3 = 6 \ \Omega \qquad R_4 = 1,5 \ \Omega \qquad U_{q1} = 24 \ V \qquad U_{q2} = 18 \ V$



Figure 2

A coil (N = 300) according to figure 3 will move with a constant speed v = 1,6 m/s through a homogeneous magnetical field (B = 1,2 T).

Calculate the maximum voltage during this movement.



Figure 3

4

The AC circuit given by figure 4 is supplied by a voltage of $u = \sqrt{2} \cdot 100 \text{ V} \cdot \cos \omega t$ with a frequency of f = 1000 Hz.

The values, indicated on the measuring instruments are: U = 100 V I = 4,6 A and P = 347 W.

Calculate the values of the resistance R_s and the capacitance C_s .





5

A very long superconducting cable with a very small diameter can carry a maximum current of I = 4000 A.

Calculate the magnetic field strength H and the magnetic flux density B for this case in a distance of 1 m and 5 m and the minimum distance to the cable where B is not less than 100 μ T.