

# NEISSE-ELEKTRO 2020

Name:

1	2	3	4	5	$\Sigma$

School:

Tasks for the finale; 90 min; with formulary (English edition)

Please use a separate sheet of paper for each task.

Write your name and school on each of these papers.

## Task 1 (24 points)

Given is the electrical circuit according to figure 1.

$$R_i = 10 \Omega$$

$$R_1 \dots R_7 = 80 \Omega$$

$$I_5 = 125 \text{ mA}$$

a) Calculate the equivalent resistance between A and B for  $R_1 \dots R_7$ .

b) Calculate all currents and voltages for all resistors.

c) Calculate the voltages  $U_{AB}$  and  $U_S$ .

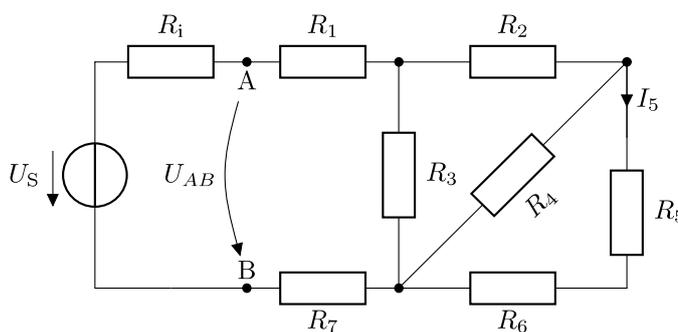


figure 1

## Task 2 (14 points)

The AC circuit given by figure 2 is supplied by a voltage of  $U_{AB} = 100\text{V}$  with a frequency of  $f = 1000 \text{ Hz}$ .

The values, indicated on the measuring instruments are:

$$U = 100 \text{ V}, \quad I = 4,6 \text{ A} \quad \text{and} \quad P = 347 \text{ W}.$$

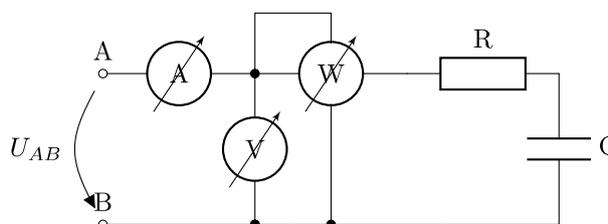


figure 2

a) Calculate the value of the resistance R.

b) Calculate the value of the capacitance C.

**Task 3** (14 points)

A sheet of paper with a thickness of  $d = 0,2 \text{ mm}$  is put into a plate capacitor (area  $A = 0,4 \text{ m}^2$ , distance  $d_1 = 1 \text{ mm}$  (vacuum), permittivity  $\epsilon_0 = 8,85 \cdot 10^{-12} \text{ As/Vm}$ ).

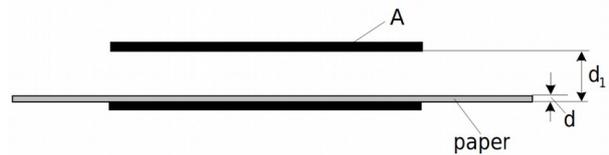


figure 3

The measured capacity is  $C = 4,0 \text{ nF}$ .

- Calculate the capacity of the paper (distance  $d$ ).
- Calculate the permittivity  $\epsilon_r$  of the paper.

**Task 4** (14 points)

A very long superconducting cable with a very small diameter can carry a maximum current of  $I = 4000 \text{ A}$ . ( $\mu_r(\text{air}) \approx \mu_r(\text{vacuum}) = 1$ )

- Calculate the magnetic field strength  $H$  and the magnetic flux density  $B$  for this case in a distance  $d$  of  $1 \text{ m}$  and  $5 \text{ m}$ .
- calculate the minimum distance  $d$  from the cable where  $B$  is less than  $100 \mu\text{T}$ .

**Task 5** (14 points)

The transformer in figure 4 has three windings. Winding  $N_0$  is connected to a source  $u_{12} = 24 \text{ Vac}$  with frequency  $f = 500 \text{ Hz}$ .

$$N_0 = 200 \quad N_1 = 30 \quad N_2 = 100$$

- Calculate the voltages  $u_{ab}$  and  $u_{cd}$ !
- A load is connected to  $u_{cd}$  and a current  $I_2 = 2 \text{ A}$  flows in winding  $N_2$ . Calculate the current in winding  $N_0$ . Calculate with efficiency  $\eta = 0,93$  and the above voltages.

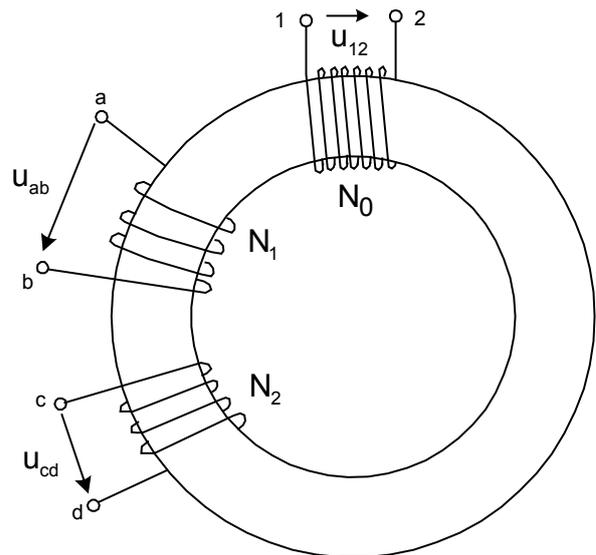


figure 4

Before end, write your **name and school on each paper**.

- until 12 o'clock, 28<sup>th</sup> march 2020: Send two photos with a **overview** of all papers with front an back side to [neisse-elektro@hszg.de](mailto:neisse-elektro@hszg.de)

- until 12 o'clock, 30<sup>th</sup> march 2020: Send a **detailed** photo or scan of **each** of your sheets to [neisse-elektro@hszg.de](mailto:neisse-elektro@hszg.de) (single or multiple emails)

See [www.hszg.de/neisse-elektro](http://www.hszg.de/neisse-elektro) → "[Vorbereitung Przygotowanie Priprava](#)" for more informations