


# NEISSE-ELEKTRO 2024

Name:

School:

1	2	3	4	5	$\Sigma$

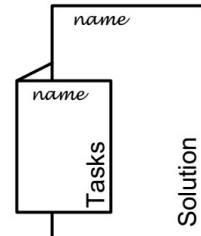Tasks for the finale; 90 min; with formulary (English edition)  
Please **use a separate sheet of paper** for each task.  
Write your name and school on **each** of these papers.  
At the end, fold your solution sheet according to the picture.



## Task 1 (20 points)

For the electrical scheme from figure 1 please calculate the following values:

- equivalent resistance  $R_0$  of the circuit
- current  $I_S$
- voltage drop  $U_R$  on resistance  $2R$

where  $R = 10\Omega$ . The voltage source  $U$  is 100V.

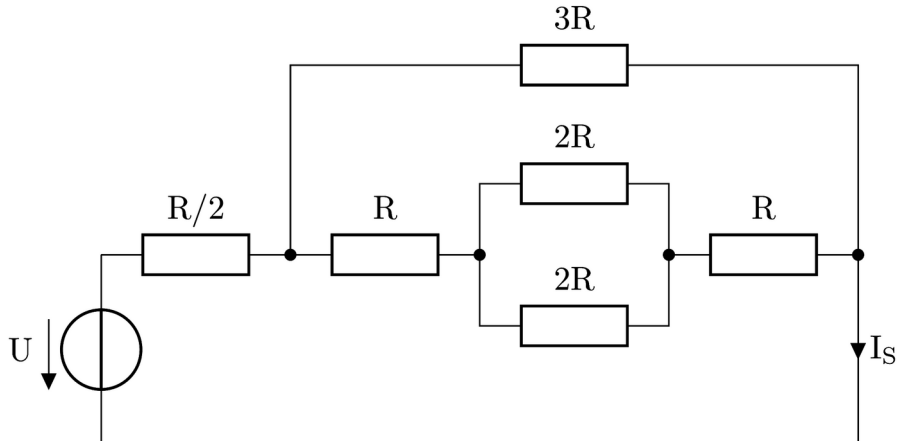


Figure 1

### Task 2 (20 points)

For a special application a real capacitor with different materials was designed. Figure 2 shows the cross section of the capacitive part only.

However, the equivalent circuit of this real capacitor includes a serial resistor  $R_s$  with low resistance value of  $0.1\text{m}\Omega$ . In addition to the capacitive part  $C$  and the series resistance  $R_s$ , a very high resistance  $R_p$  of  $10\text{M}\Omega$  in parallel should be taken into account.

Relative permittivities:  $\epsilon_{r1} = 5,000$ ,  $\epsilon_{r2} = 2000$ ,  $\epsilon_{r3} = 3000$ ,  $\epsilon_{r4} = 2200$   
Distances:  $d_1 = 5 \cdot 10^{-12}\text{m}$ ,  $d_2 = 2 \cdot 10^{-11}\text{m}$ ,  $d_3 = 3 \cdot 10^{-11}\text{m}$   
Surface area  $S = 0,1129\text{m}^2$

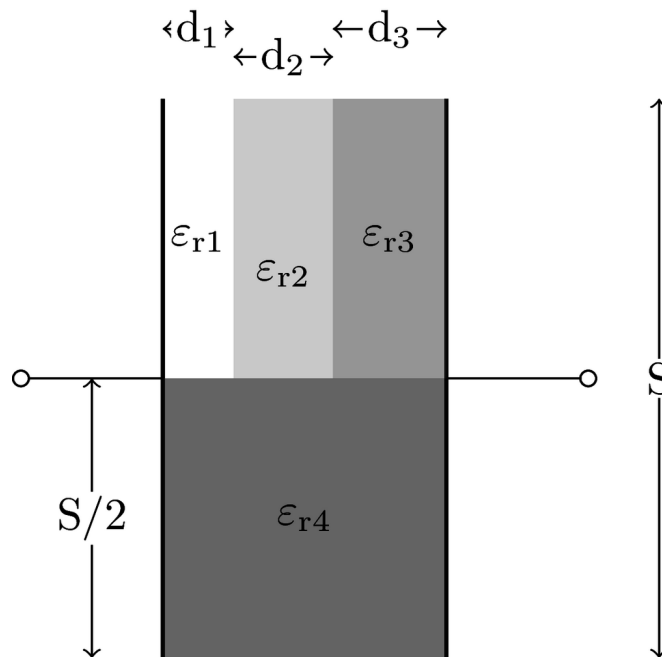


Figure 2

- Draw the equivalent circuit with all elements.
- Calculate the capacitance for each capacitor.
- Calculate the total capacitance of the construction.
- Calculate total charge if the DC voltage at terminals of the real capacitor is  $100\text{V}$  in steady state (after long time).
- Calculate the resistance of the total capacitance for the nominal frequency of  $50\text{Hz}$ .

### Task 3 (20 points)

Given is a node with three currents (figure 3a). Two currents are known with their value over time (figure 3b).

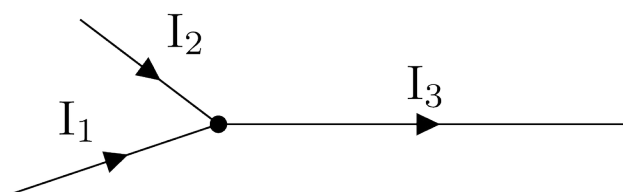


Figure 3a

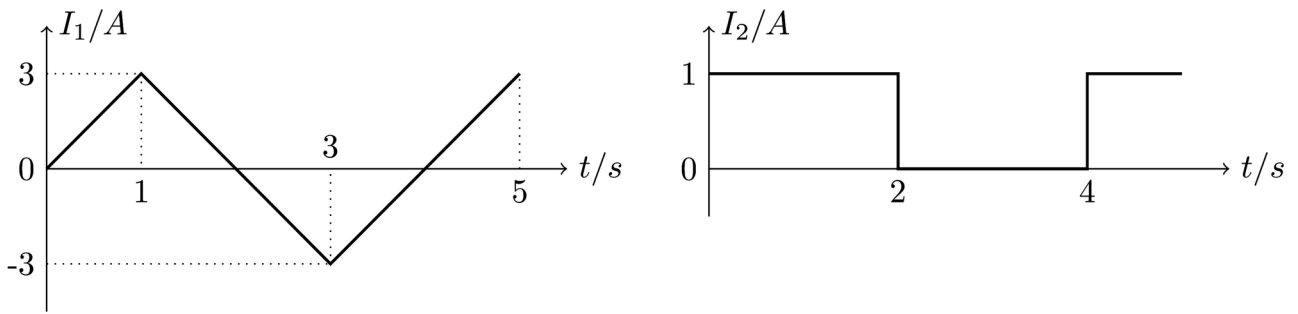


Figure 3b

- Draw the current  $I_3$  over the time. Mark the maximum and minimal current in your sketch
- Calculate the values from a).
- For the wire with current  $I_3$ : draw the value of the magnetic flux density  $B$  at a distance  $r = 0,01\text{cm}$  caused by  $I_3$  over time. Assume a infinite long wire. Mark the maximum and minimal values.
- Calculate maximum and minimum value of flux density of c).

#### Task 4 (20 points)

Given is a transformer with an AC input voltage  $U_{in} = 230\text{V}$  with  $N_p = 400$  windings on the primary high voltage side and two secondary windings with  $N_{s1} = 20$  and  $N_{s2} = 40$ .

The thermal losses in magnetic core of transformer are reflected by resistance  $R_{Mp} = 10\text{k}\Omega$ . The thermal losses of the windings of secondary sides are reflected by  $R_{s1} = 0,5\Omega$ , and  $R_{s2} = 1\Omega$  respectively.

Both outputs of the transformer are connected with LED lamps with nominal power  $P_{n1} = 5\text{ W}$  (at  $U_{n1} = 12\text{V}$ ) and  $P_{n2} = 10\text{ W}$  (at  $U_{n2} = 24\text{ V}$ ). Assume the LEDs as fixed value resistors for your calculations.

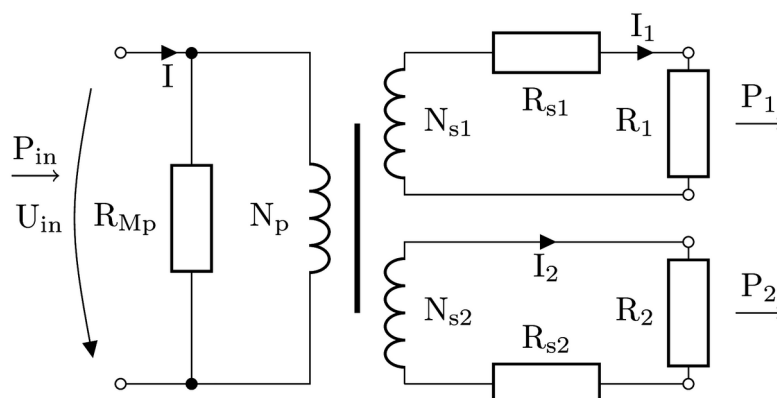


Figure 4

- Please calculate the current  $I$  on the primary side
- Calculate the power  $P_{in}$  on the primary side
- Calculate the effectiveness of this circuit during parallel operation of both LEDs.

**Task 5** (20 points)

A metal wire is moving in direction of the DC source  $U = 3,5\text{V}$  with the constant speed of  $v=36\text{ km/h}$  on two parallel infinite long busbars with distance to each other of  $d=1,5\text{m}$  (see figure 5). The resistance of the busbar is neglected. The constant magnetic flux density  $B=0,1\text{T}$  occurs in this area. Please calculate:

- the induction voltage due to movement of the wire
- current flowing in the circuit
- generated power needed to guarantee the movement with constant speed  $v$  (remark: in kinetics, the power is reflected as  $|P|=|F \cdot v|$ )

The resistance of the wire is  $R_{\text{WIRE}} = 0,1\Omega$  and resistance of the source  $R$  is  $0,4\Omega$ .

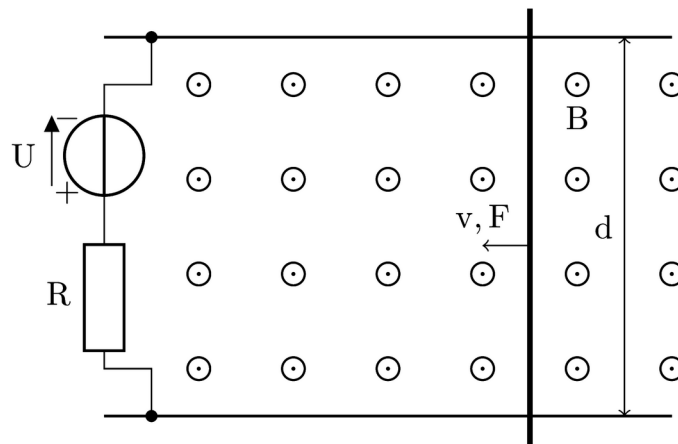


Figure 5