

NEISSE-ELEKTRO 2021

Exercise #2 - Capacitors, Charges


Official formula sheet: hszg.de/neisse-elektro --> [Aufgaben](#) --> [formula sheet2019.pdf](#)

1) A current of 1mA flows into a capacitor for 1 second. Calculate the increased value of the voltage for an capacitor A with $C_A = 10\mu\text{F}$. Which capacitor would be charged to 15V with the same current and time?

2) Calculate the capacitance of a capacitor with two plates with the area of A4 paper (210 mm x 297 mm). The distance between is 0.3 mm and filled with air. Calculate the capacitance if you fill the gap with fluid ($\epsilon_r=3.5$).

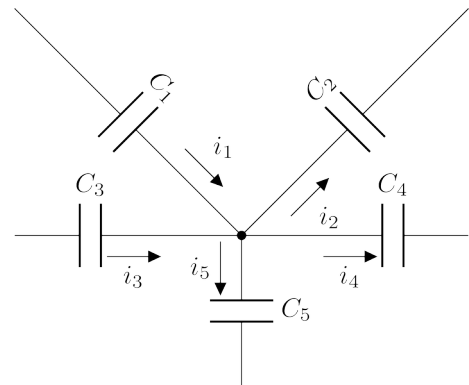3) You see a part of a circuit. Calculate the current i_5 of capacitor 5:

$C_1=1\mu\text{F}$, $i_1=1\text{mA}$, $C_2=2\mu\text{F}$, $i_2=0.5\text{mA}$, $C_3=4\mu\text{F}$, $i_3=0.25\text{mA}$,
 $C_4=0.1\mu\text{F}$, $i_4=10\text{mA}$, $C_5=10\mu\text{F}$



4) Without knowledge of the context of the formulas, can you explain why at least one formula seems wrong?

$$(a) f = \frac{1}{2\pi\sqrt{L_1 C_1 C_2 C_3}} \quad (b) f = \frac{1}{2\pi\sqrt{L_1 (C_1 + C_2 + C_3)}}$$

$$(c) f = \frac{1}{2\pi\sqrt{L_1 \left(C_3 + \frac{C_1 C_2}{C_1 + C_2} \right)}} \quad (d) f = \frac{1}{2\pi\sqrt{L_1 \left(\frac{C_1 C_2 C_3}{C_2 C_3 + C_1 C_3 + C_1 C_2} \right)}}$$

5) A capacitor $C=1500\mu\text{F}$ in a photovoltaic inverter is charged to a voltage of 750V. If it is switched off it gets discharged by a resistor. Calculate the value of the resistor, that after a time of 3 min the voltage drops below 40V.


6) Calculate the capacitance.

$a = b = 10\text{cm}$
 $a_1 = 4\text{cm}$

$d = 5\text{mm}$
 $d_1 = 2\text{mm}$

$\epsilon_0 = 8.85 \cdot 10^{-12} \text{ As/Vm}$

glas: $\epsilon_r = 6$

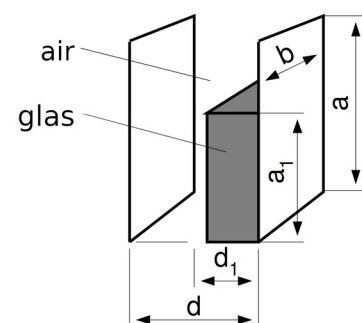

You are invited to work on a collaborative document for the solution:

<https://pad.gwdg.de/OedZi2wnQFi1BHsG7RQGMw>

<https://hszg.de/neisse-elektro> Egmont Schreiter et al.

Licence of this document and all contributions: [OER Open Educational Ressources](#), [CC-BY-SA 4.0](#),